

Electric Circuits (I) (Final Exam)

Department of Electrical Engineering, National Cheng Kung University

Date: Jan. 17, 2018

1. Refer to **Fig.1**. Express $i(t)$ in terms of singularity functions. (14pts)

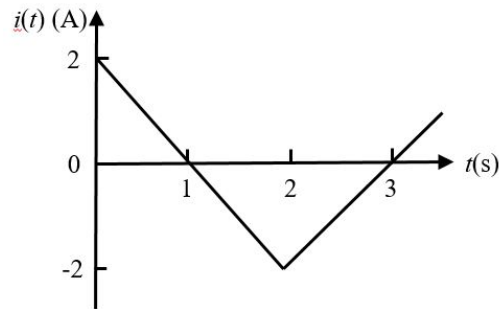


Fig.1

2. Determine $v(t)$ for $t > 0$ in the circuit of **Fig.2** if $v(0) = 0$. (14pts)

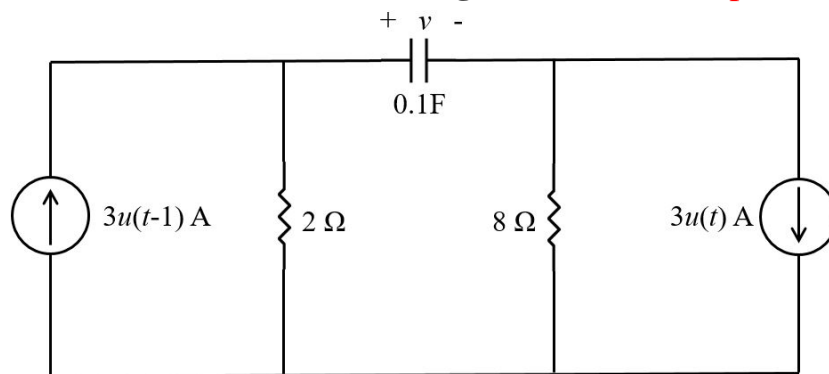


Fig.2

3. The switch in the circuit shown in **Fig.3** has been closed for a long time before it is opened at $t = 0$. Find (a) $i_L(t)$ for $t \geq 0$, (b) $i_o(t)$ for $t \geq 0^+$, (c) $v_o(t)$ for $t \geq 0^+$, (d) the power dissipated in the 10Ω resistor. (18pts)

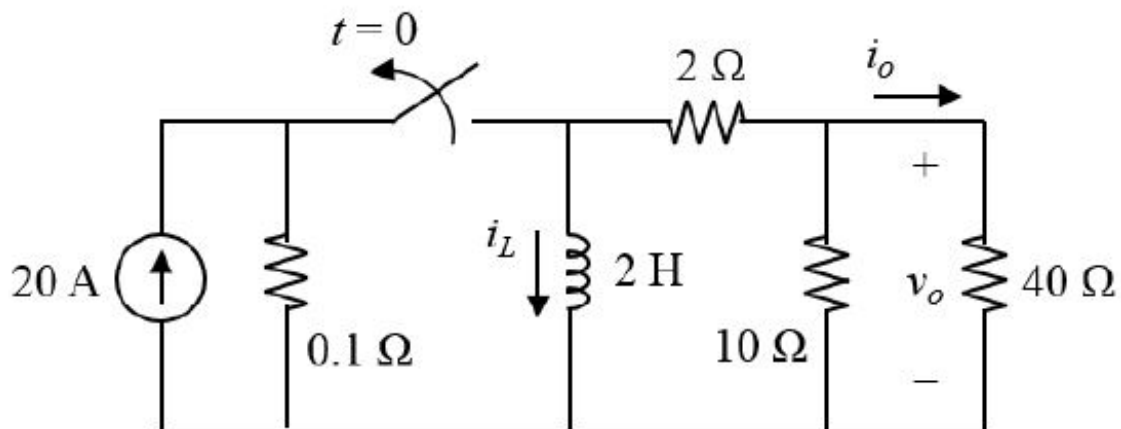


Fig.3

4. No energy is stored in the 0.1H inductor or the $0.4\text{ }\mu\text{F}$ capacitor when the switch in the circuit shown in **Fig. 4** is closed. Find $v_C(t)$ for $t \geq 0$. (18pts)

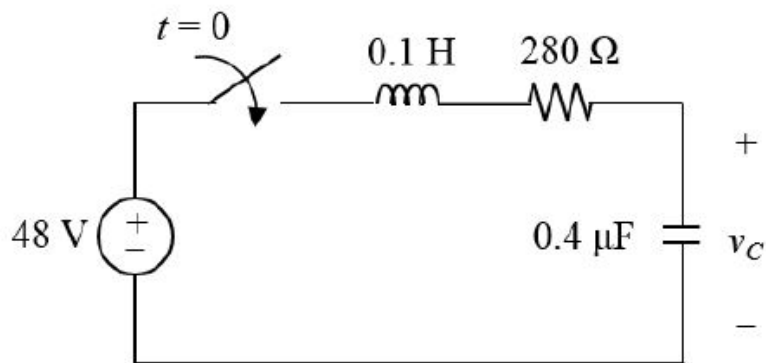


Fig.4

5. Assuming that the switch in **Fig. 5** has been in position A for a long time and is moved to position B at $t = 0$. Find $v(t)$ for all $t \geq 0$. (18pts)

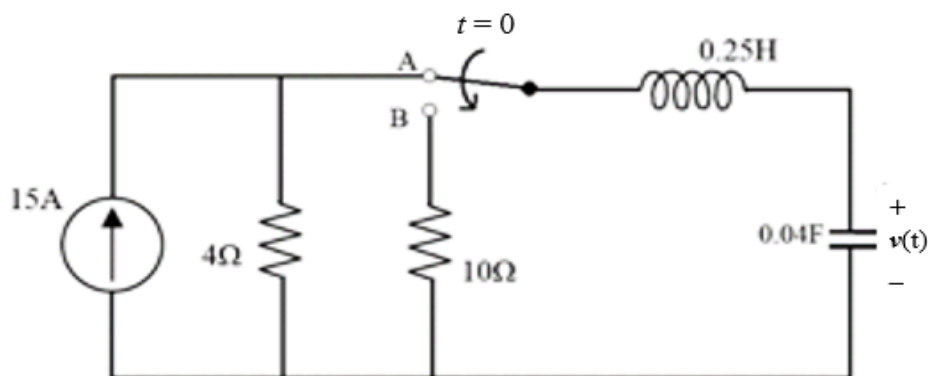


Fig.5

6. In the op amp circuit of **Fig.6**, determine $v_o(t)$ for $t > 0$. Let $v_s(t) = u(t)$. (18pts)

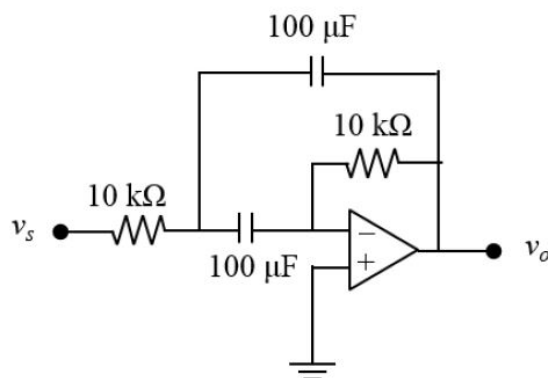


Fig.6