


電磁作業工 謝東翰 14284028

Problem 6

[Using Smith chart] Given a series RC load with an impedance $Z_L = 200 - j100 \Omega$ and to a 75Ω , 0.7λ transmission line at a frequency of 500 MHz . "Use Smith chart" to evaluate (describe all the steps in details): (a) VSWR and the reflection coefficient at input of the line, (b) the input impedance Z_{in} looking into this line and its corresponding Y_{in} at the input, (c) the distance of first voltage minimum from the load, (d) inserted a shunt short-circuited stub at the load to make a "real" reflection coefficient (no imaginary part), find the minimum required length of the stub section and (e) the corresponding VSWR.

Answers:

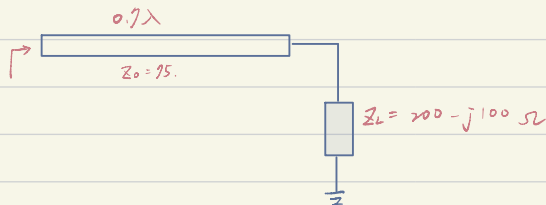(a) $VSWR = 3.42$; $\Gamma_{in} = \dots$ (b) $Z_{in} = \dots - j10.4 \Omega$; $Y_{in} = \dots$;
(c) 0.224λ ; (d) \dots ; (e) $VSWR = 10/3$



- a. $1^\circ z_n = \frac{Z_L}{Z_0} = \frac{200 - j100}{75} = 2.67 - 1.33j \Rightarrow P_1(2.67, -1.33j)$
 2° By smith chart: 以 P_1 為圓心, OP_1 為半徑的圓交右軸於 $\begin{cases} S_1(3, 0) \\ S_2(0.34, 0) \end{cases}$
 $\therefore VSWR = 3.4$
 $0.275\lambda + 0.7\lambda \Rightarrow 0.475\lambda + 0.5\lambda$
 3° By smith chart: O 連線至 l_2 處, 交 $P_2 \Rightarrow P_2 = \overline{OP_2} \angle 160.3^\circ$
 4° From 比例 $R: \overline{OP_2} = 0.54 \Rightarrow \underline{P_{in} = 0.54 \angle 160.3^\circ}$

- b. $1^\circ P_2(0.34, -0.15) \Rightarrow Z_{in} = Z_0(0.34, -0.15) = 25.5 - j11.25 (\Omega)$
 2° By smith chart: $P_3(2.7, 1.1) \Rightarrow \underline{Y_{in} = (2.7 + j1.1) Z_0 = 202.5 + 82.5j (\Omega)}$

c. $0.5\lambda - 0.275\lambda = 0.225\lambda$

- d. By smith chart: $P_4(0.34, 0.15) \Rightarrow Y = (0.34, 0) = \overline{OP_4} + (0, -0.15)$
 length of $-j0.15 = 0.475 \Rightarrow d_{min} = 0.475\lambda - 0.25\lambda = 0.225\lambda$
 shunt stub 提供 $-j0.15$

e. $VSWR(-0.7\lambda) = \frac{|1 + \Gamma(-0.7\lambda)|_{max}}{|1 - \Gamma(-0.7\lambda)|_{min}} = \frac{1}{0.3} = \frac{10}{3}$

\downarrow
 $\frac{1 + |\Gamma|}{1 - |\Gamma|}$