

E14082(18) 蘇品瑄

電 I 2nd 期中

$$1. \frac{V_{out}}{V_{in}} = \frac{\frac{R_2 R_3}{R_2 + R_3} + Z_L + Z_{C1+C2}}{R_1 + (\frac{R_2 R_3}{R_2 + R_3} + Z_L + Z_{C1+C2})} = \frac{(\frac{200^2}{400} + 4j\omega + \frac{1}{10^{-4}j\omega}) \times 400 \times 10^{-4}j\omega}{[300 + (\frac{200^2}{400} + 4j\omega + \frac{1}{10^{-4}j\omega})] \times 400 \times 10^{-4}j\omega} \quad [C_1 + C_2 = (20 + 80) \times 10^{-6} = 10^{-4}]$$

$$= \frac{4j\omega - 0.16\omega^2 + 400}{12j\omega + 4j\omega - 0.16\omega^2 + 400} = \frac{(-0.16\omega^2 + 400) + j(4\omega)}{(-0.16\omega^2 + 400) + j(16\omega)} \quad \#$$

$$2. \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.5 \times 0.1}} = 4.472 \text{ rad/s} \quad \#$$

$$B = \frac{\omega_0}{Q} = \omega_0^2 RC = \frac{R}{L} = \frac{4}{0.5} = 8 \text{ rad/s} \quad \#$$

$$3. \text{Thévenin: } v_T \quad I_T = \frac{v_T}{R_T}$$

$$\text{Norton: } I_N \quad R_N$$

$$I_N = I_T = \frac{v_T}{R_T} \Rightarrow v_T = I_N R_T = I_N R_N \Rightarrow R_T = R_N$$

4. ① Remove the loading

② Zero all voltage or current source

③ Compute the total resistance between load terminals with the load removed.

Thévenin Voltage:

$$v_s \text{ source, } R_1, R_2, R_3, R_4, R_0 \Rightarrow v_T = v_{R_2} = v_s \times \frac{R_2}{R_1 + R_2} \quad \#$$

Norton Current:

$$v_s \text{ source, } R_1, R_2, R_3, R_4, R_0 \Rightarrow \begin{cases} v_s - R_1 \bar{v}_1 - R_2 (\bar{v}_1 - \bar{v}_2) = 0 & \text{--- ①} \\ -R_2 (\bar{v}_2 - \bar{v}_1) - R_3 \bar{v}_2 = 0 \Rightarrow \bar{v}_1 = \frac{R_2 + R_3}{R_2} \bar{v}_2 & \text{--- ②} \end{cases}$$

③ 代入 ①


$$v_s = \frac{(R_1 + R_2)(R_2 + R_3)}{R_2} \bar{v}_2 - R_2 \bar{v}_2 = \left[\frac{(R_1 + R_2)(R_2 + R_3)}{R_2} - R_2 \right] \bar{v}_2$$

$$\bar{v}_N = \bar{v}_2 = \frac{v_s R_2}{(R_1 + R_2)(R_2 + R_3) - R_2^2} = \frac{v_s R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} \quad \#$$

Equivalent resistance:

$$v_s \text{ source, } R_1, R_2, R_3, R_4, R_0 \Rightarrow R_{eq} = [(R_1 \parallel R_2) + R_3] \parallel R_4 \quad \#$$

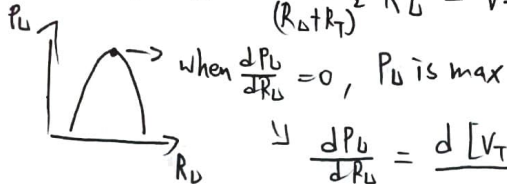6. $P_L = I_L^2 R_L = \frac{V_T^2}{(R_L + R_T)^2} R_L = V_T^2 (R_L + R_T)^{-2} R_L$



$$\Rightarrow \frac{dP_L}{dR_L} = \frac{d[V_T^2 (R_L + R_T)^{-2} R_L]}{dR_L} = V_T^2 (-2)(R_L + R_T)^{-3} R_L + V_T^2 (R_L + R_T)^{-2}$$

$$= V_T^2 (R_L + R_T)^{-2} [-2(R_L + R_T)^{-1} R_L + 1] = 0$$


$$\Rightarrow 1 = 2 \frac{R_L}{R_L + R_T}$$

$$\Rightarrow R_L + R_T = 2 R_L$$


$$\Rightarrow R_T = R_L$$

11 $\frac{dP_L}{dR_L} = 0$ when $R_L = R_T = R_N \#$

9. (a) $v_s(t) = A \cos \omega t$

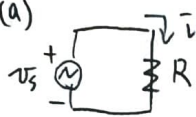
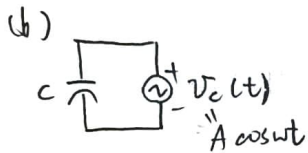
$$\begin{cases} V_s(j\omega) = A e^{j0^\circ} \\ I_s(j\omega) = \frac{A}{R} e^{j0^\circ} \end{cases} \Rightarrow Z_R(j\omega) = \frac{V_s(j\omega)}{I_s(j\omega)} = R \#$$



$$i_c(t) = C \frac{dv_c(t)}{dt} = C [-A\omega \sin(\omega t)] = \omega C A \cos(\omega t + 90^\circ)$$


$$Z_C(j\omega) = \frac{V_C(j\omega)}{I_C(j\omega)} = \frac{A e^{j0^\circ}}{\omega C A e^{j90^\circ}} = \frac{1}{\omega C} e^{-j90^\circ} = -j \frac{1}{\omega C} = \frac{1}{j\omega C} \#$$



$$i_L(t) = \frac{1}{L} \int A \cos \omega t dt = \frac{A}{L} \frac{\sin \omega t}{\omega} = \frac{A}{\omega L} \cos(\omega t - 90^\circ)$$

$$Z_L(j\omega) = \frac{V_L(j\omega)}{I_L(j\omega)} = \frac{A e^{j0^\circ}}{\frac{A}{\omega L} e^{-j90^\circ}} = \omega L e^{j90^\circ} = j\omega L \#$$


1. ① low-pass filter

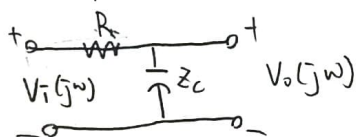

low $\omega \Rightarrow C$ 断路 \Rightarrow 过

high $\omega \Rightarrow C$ 短路 \Rightarrow 挡


② high-pass filter

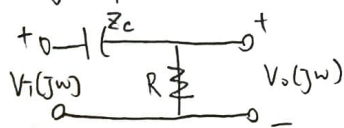

low $\omega \Rightarrow C$ 断路 \Rightarrow 挡

high $\omega \Rightarrow C$ 短路 \Rightarrow 过


③ Band-pass filter

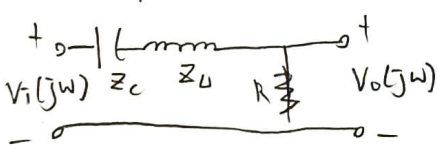

low $\omega \Rightarrow \begin{cases} C \text{ 断路} \\ L \text{ 短路} \end{cases} \Rightarrow$ 挡

high $\omega \Rightarrow \begin{cases} C \text{ 短路} \\ L \text{ 断路} \end{cases} \Rightarrow$ 挡


④ Notch filter

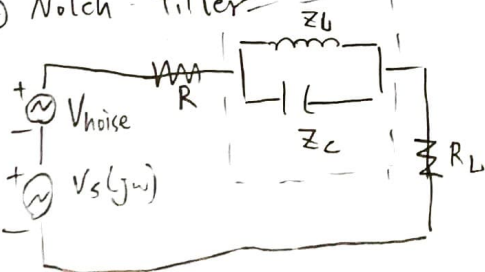

low $\omega \Rightarrow \begin{cases} C \text{ 断路} \\ L \text{ 短路} \end{cases} \Rightarrow$ 过

high $\omega \Rightarrow \begin{cases} C \text{ 短路} \\ L \text{ 断路} \end{cases} \Rightarrow$ 过

8. ① low-pass filter

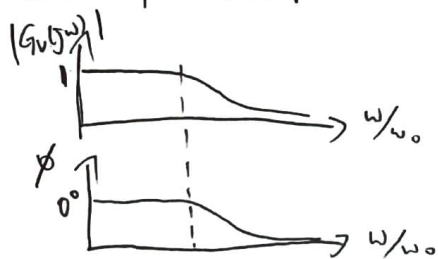


$|G_v|$ must be 1
 low $\omega \Rightarrow \phi$ must be 0° , so that there won't have noise in $|G_v(j\omega)|$
 high $\omega \Rightarrow \phi$ can be any number, because $|G_v(j\omega)|$ would be zero.

② high-pass filter




low $\omega \Rightarrow \phi$ can be any number, because $|G_v(j\omega)|$ would be zero.
 high $\omega \Rightarrow \phi$ must be 0° , so that there won't have noise in $|G_v(j\omega)|$.
 $|G_v|$ must be 1

③ Band-pass filter

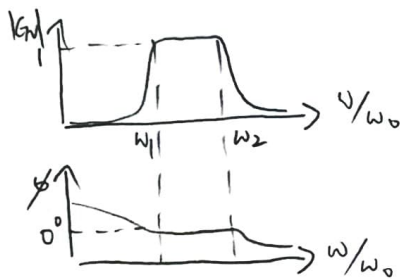


$|G_v|$ must be 1
 $\omega_1 < \omega < \omega_2 \Rightarrow \phi$ must be 0° , so that there won't have noise in $|G_v|$.
 $\omega < \omega_1$
 $\omega > \omega_2 \Rightarrow \phi$ can be any number, because $|G_v(j\omega)|$ would be zero.

④ Notch filter

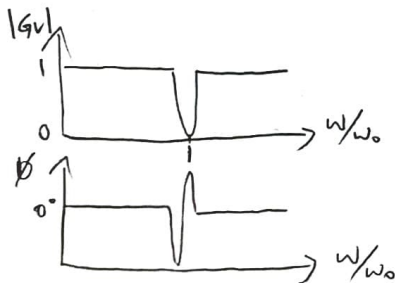

$\omega = \omega_0 \Rightarrow \phi$ can be any number, because $|G_v|$ would be zero.
 $\omega \neq \omega_0 \Rightarrow \phi$ must be 0° , so that there won't have noise in $|G_v|$.
 $|G_v|$ must be 1

10.

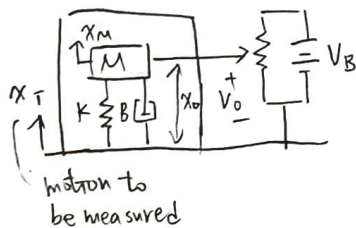

$$k x_o + B \frac{dx_o}{dt} = M \frac{d^2 x_M}{dt^2} \quad \underline{x_M = x_i - x_o} \quad M \left(\frac{d^2 x_i}{dt^2} - \frac{d^2 x_o}{dt^2} \right)$$

$$\begin{cases} x_i(j\omega) = |x_i| e^{j\phi_i} \\ x_o(j\omega) = |x_o| e^{j\phi_o} \end{cases}$$

$$M(j\omega)^2 x_o + B(j\omega) x_o + k x_o = M(j\omega)^2 x_i$$

$$\Rightarrow (-\omega^2 M + j\omega B + k) x_o = -\omega^2 M x_i$$

$$\Rightarrow \frac{x_o(j\omega)}{x_i(j\omega)} = \frac{-\omega^2 M}{-\omega^2 M + j\omega B + k}$$