

P6.16

From Figure P6.16, we see that the period of the signals is 10 ms. Therefore, the frequency is 100 Hz. Because the input reaches a positive peak at $t = 2$ ms, it has a phase angle of

$$\theta_{\text{in}} = -(t_d / T) \times 360^\circ = -(2 / 10) \times 360^\circ = -72^\circ$$

The output reaches its peak at 4 ms, and its phase angle is

$$\theta_{\text{out}} = -(t_d / T) \times 360^\circ = -(4 / 10) \times 360^\circ = -144^\circ$$

The transfer function is

$$H(100) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{2 \angle -144^\circ}{1 \angle -72^\circ} = 2 \angle -72^\circ$$

P6.25*

The half-power frequency of the filter is

$$f_B = \frac{1}{2\pi RC} = 500 \text{ Hz}$$

The transfer function is given by Equation 6.9 in the text:

$$H(f) = \frac{1}{1 + j(f/f_B)}$$

The given input signal is

$$v_{\text{in}}(t) = 5 \cos(500\pi t) + 10 \cos(1000\pi t - 30^\circ) + 15 \cos(2000\pi t + 60^\circ)$$

which has components with frequencies of 250, 500, and 1000 Hz.

Evaluating the transfer function for these frequencies yields:

$$H(250) = \frac{1}{1 + j(250/500)} = 0.8944 \angle -26.57^\circ$$

$$H(500) = 0.7071 \angle -45^\circ$$

$$H(1000) = 0.4472 \angle -63.43^\circ$$


Applying the appropriate value of the transfer function to each component of the

input signal yields the output:

$$v_{out}(t) = 4.472 \cos(500\pi t - 26.57^\circ) + 7.071 \cos(1000\pi t - 75^\circ) + 6.708 \cos(2000\pi t + 3.43^\circ)$$

P6.30*

The circuit seen by the capacitance is:

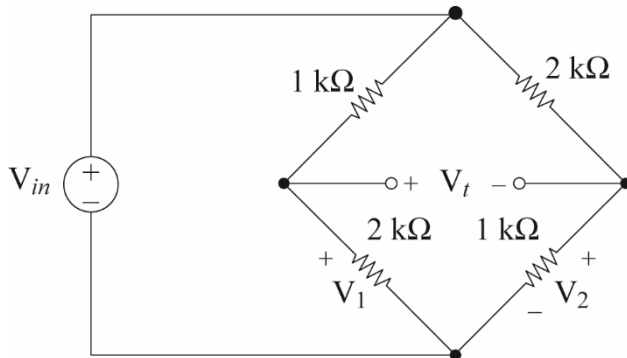


The open-circuit or Thévenin voltage is

$$\begin{aligned} V_t &= V_1 - V_2 \\ &= V_{in} \frac{2000}{2000 + 1000} - V_{in} \frac{1000}{1000 + 2000} \end{aligned}$$

Thus, we obtain:

$$V_t = \frac{1}{3} V_{in} \quad (1)$$


Zeroing the source, we have

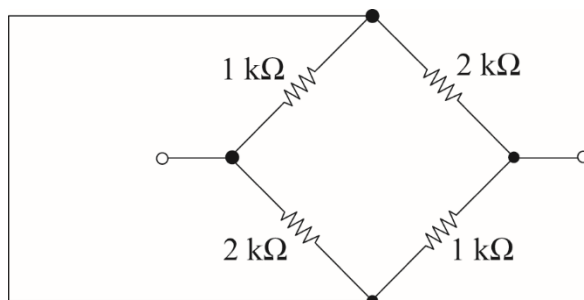

The Thévenin resistance is

$$R_t = \frac{1}{1/1000 + 1/2000} + \frac{1}{1/2000 + 1/1000}$$

Thus, the equivalent circuit is:

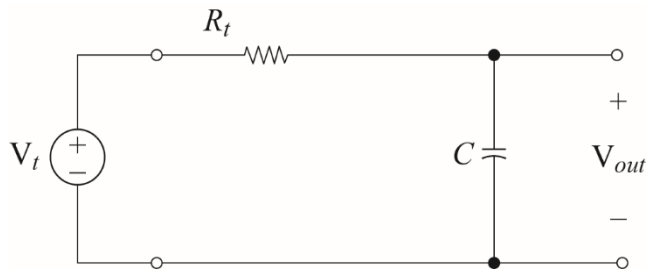

As in the text, this circuit has the transfer function:


$$\frac{V_{out}}{V_t} = \frac{1}{1 + j(f/f_B)} \quad (2)$$

$$\text{where } f_B = \frac{1}{2\pi R_t C} = \frac{1}{2\pi 1333 \times 10^{-5} \times 2} = 5.97 \text{ Hz}$$

Using Equation (1) to substitute for V_t in Equation (2) and rearranging, we have

$$\frac{V_{out}}{V_{in}} = \frac{1/3}{1 + j(f/f_B)}$$

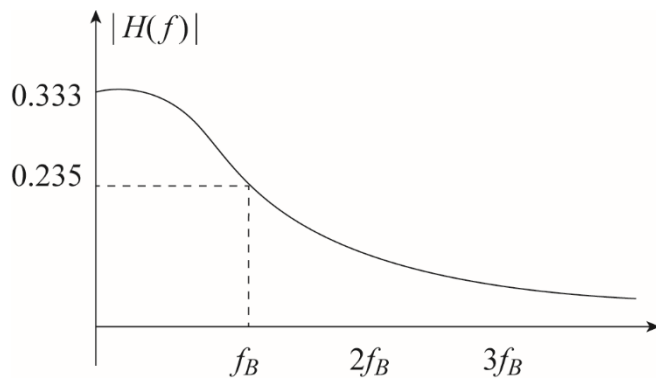A sketch of the transfer-function magnitude is:



P6.46*

(a) The overall transfer function is the product of the transfer

functions of the filters in cascade:

$$H(f) = H_1(f) \times H_2(f) = \frac{1}{[1 + j(f/f_B)]^2}$$

$$\begin{aligned}
 (b) \quad |H(f)| &= \frac{1}{1 + (f/f_B)^2} \\
 |H(f_{3dB})| &= \frac{1}{\sqrt{2}} = \frac{1}{1 + (f_{3dB}/f_B)^2} \\
 (f_{3dB}/f_B)^2 &= \sqrt{2} - 1 \\
 f_{3dB} &= f_B \sqrt{\sqrt{2} - 1} = 0.6436 f_B
 \end{aligned}$$

P6.57


First, we find the Thévenin equivalent for the source and the resistances. The Thévenin resistance is

$$R_t = \frac{1}{1/R_1 + 1/R_2} = 900 \, \Omega$$

and the Thévenin voltage is

$$V_t = \frac{R_2}{R_1 + R_2} V_{in} = 0.1 V_{in}$$

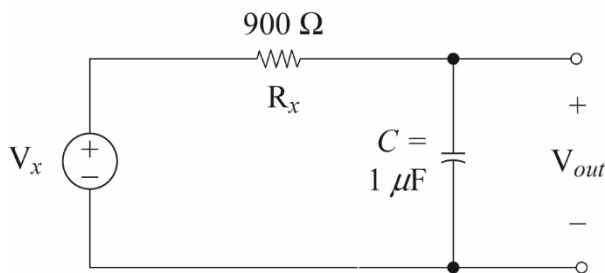Thus, an equivalent for the original circuit is:




This is a lowpass filter having a transfer function given by Equation 6.8 (with changes in notation):

$$\frac{V_{out}}{V_t} = \frac{1}{1 + j(f/f_B)}$$

where $f_B = 1/(2\pi R_t C) = 8.84 \text{ Hz}$.

Using the fact that $V_t = 0.1 V_{in}$, we have $H(f) = \frac{V_{out}}{V_{in}} = \frac{0.1}{1 + j(f/f_B)}$

The Bode plots are:

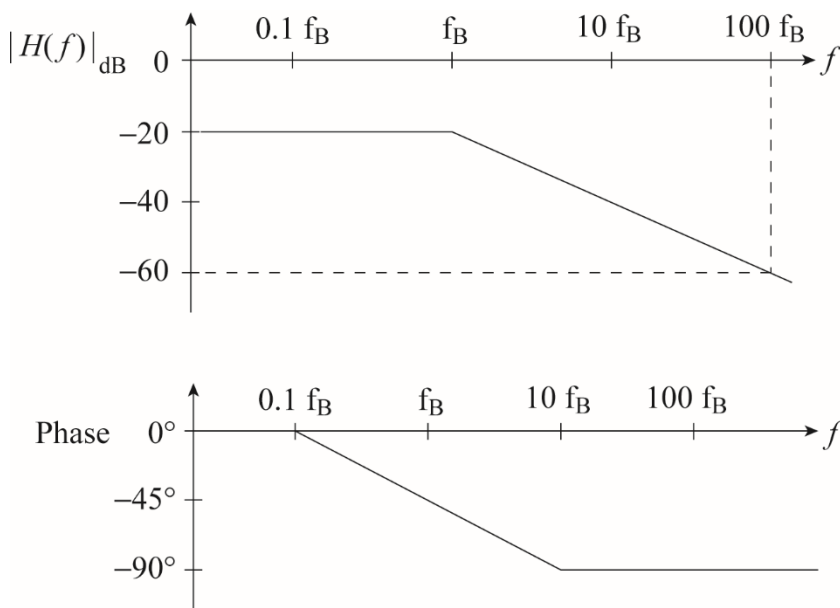

P6.65*

The input signal is given by

$$v_{in}(t) = 10 + 15\cos(2000\pi t)$$

This signal has components at $f = 0 \text{ Hz}$ and $f = 1000 \text{ Hz}$. The transfer-function values at these frequencies are:

$$H(0) = \frac{j0}{1 + j0} = 0$$

$$H(1000) = \frac{j1}{1 + j1} = 0.7071 \angle 45^\circ$$

Applying these transfer-function values to the respective components yields:

$$v_{out}(t) = 10.60\cos(2000\pi t + 45^\circ)$$